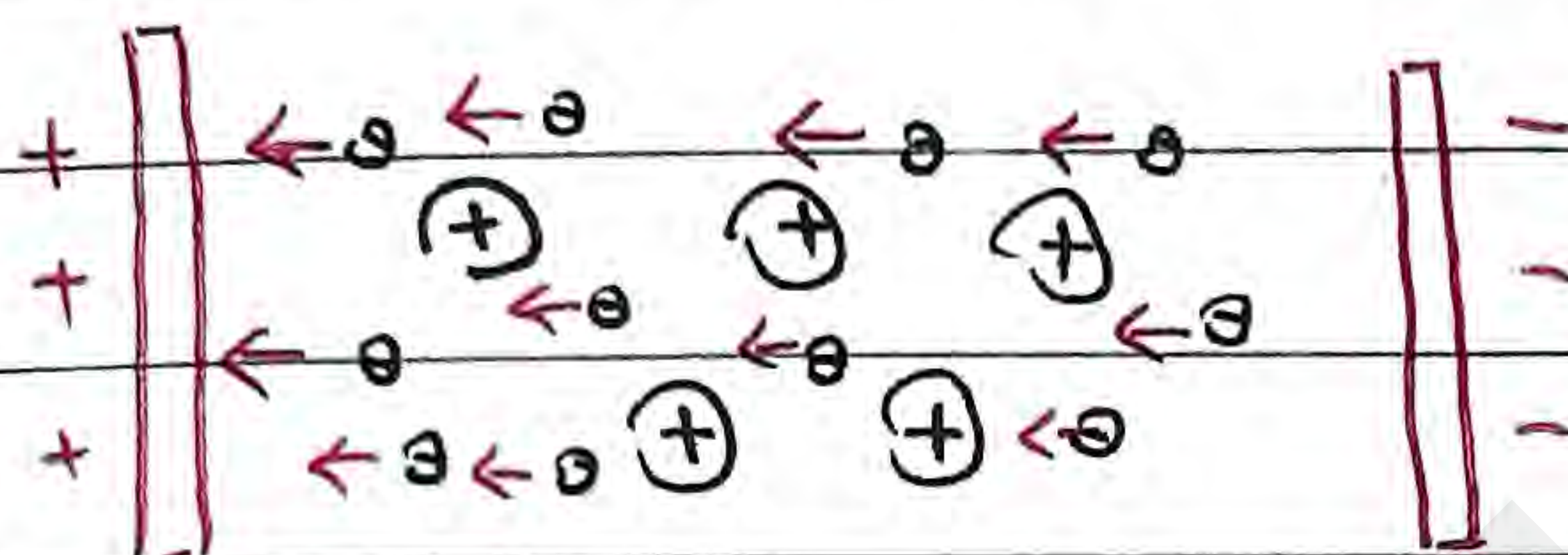


Electric current

When do charges move?

- When there's a force exerted on the charge
- In other words, when there's an electric field

Let's consider a lattice structure



Let's add
a uniform electric
field

Adding a uniform electric field means, probabilistically, most electrons flow in the same direction

- Only electrons move because of lattice structure (more energetically favorable)

* Electrons do not move linearly due to electron-electron repulsion and electron-nucleus attraction. It's more zig-zag than linear.

The direction of electric current is defined as that opposite to the motion of electrons

$$\begin{array}{c} \leftarrow e \leftarrow e \\ \hline \rightarrow \\ I = \text{electric current} \end{array}$$


Electrons also move really slowly (10^{-2} m s^{-1} magnitude)

• However, electricity is instant due to fields, which instantly exert force on e^-

Electric current

Defined as change in charges per reference area in a given time unit (second)

$$I = \frac{\Delta q}{\Delta t}$$

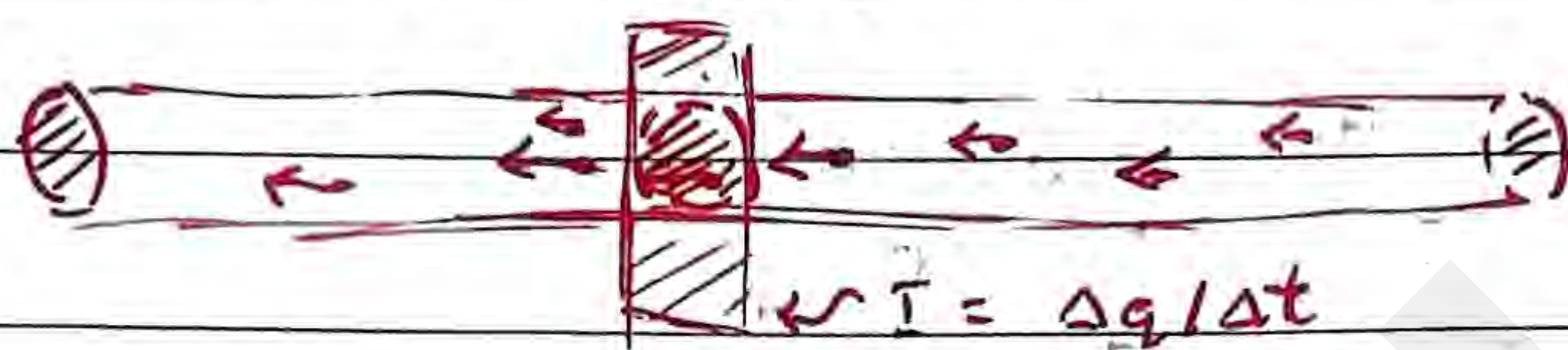


where units are $C \cdot s^{-1} = A = \text{Ampere}$

Electric resistance

While friction certainly does not exist in a subatomic level, there's repulsive and resistive forces against electrons.

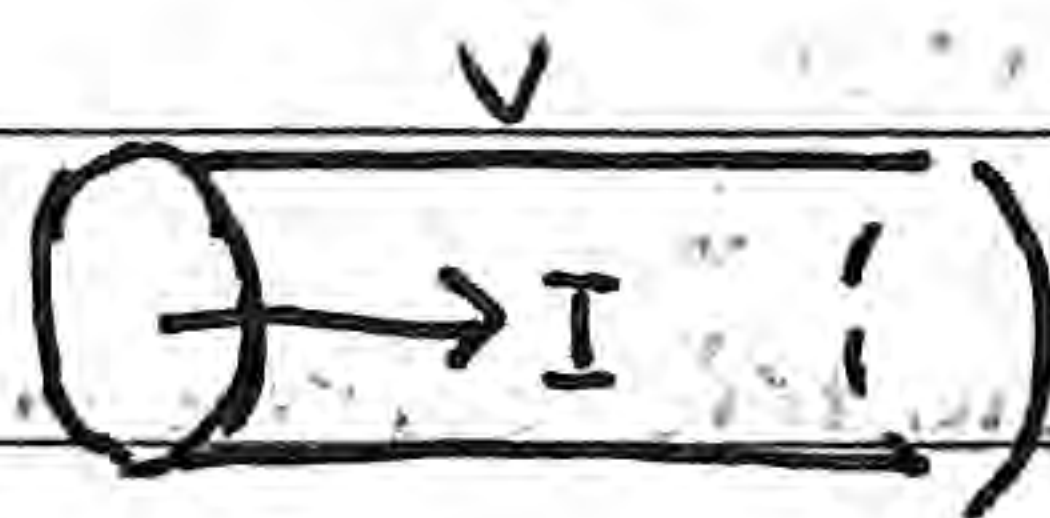This is known as resistance, defined as the potential difference over the current in a given conductor




$$R = \frac{V}{I} [V \cdot A^{-1} = \Omega = \text{Ohm}]$$

Electric resistance

When you measure current per different values of voltage, you can calculate the resistance of the material upon a change in voltage (applied)


- Graphing them out:

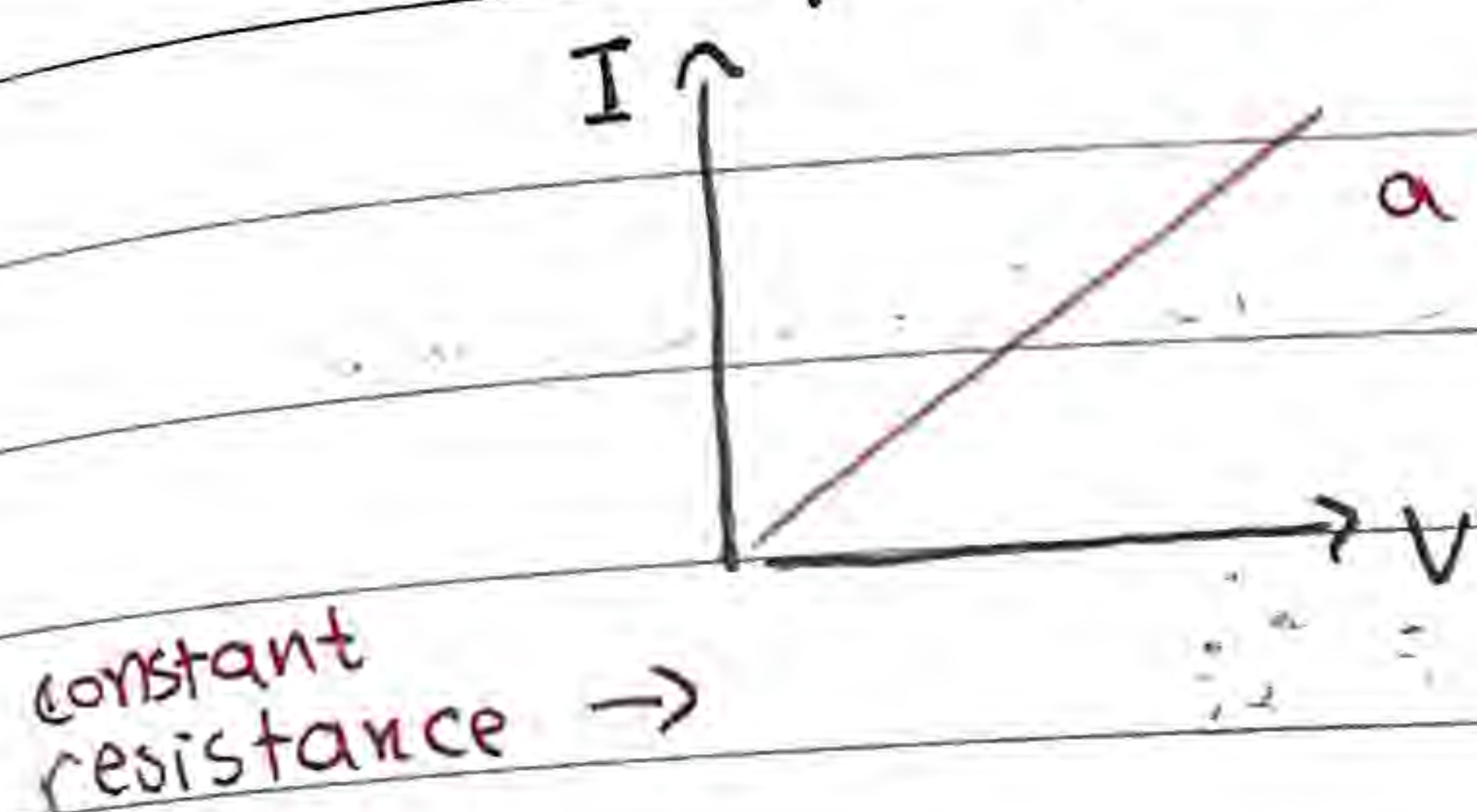

a perfectly linear relation

This is an ohmic material
(e.g. resistors)

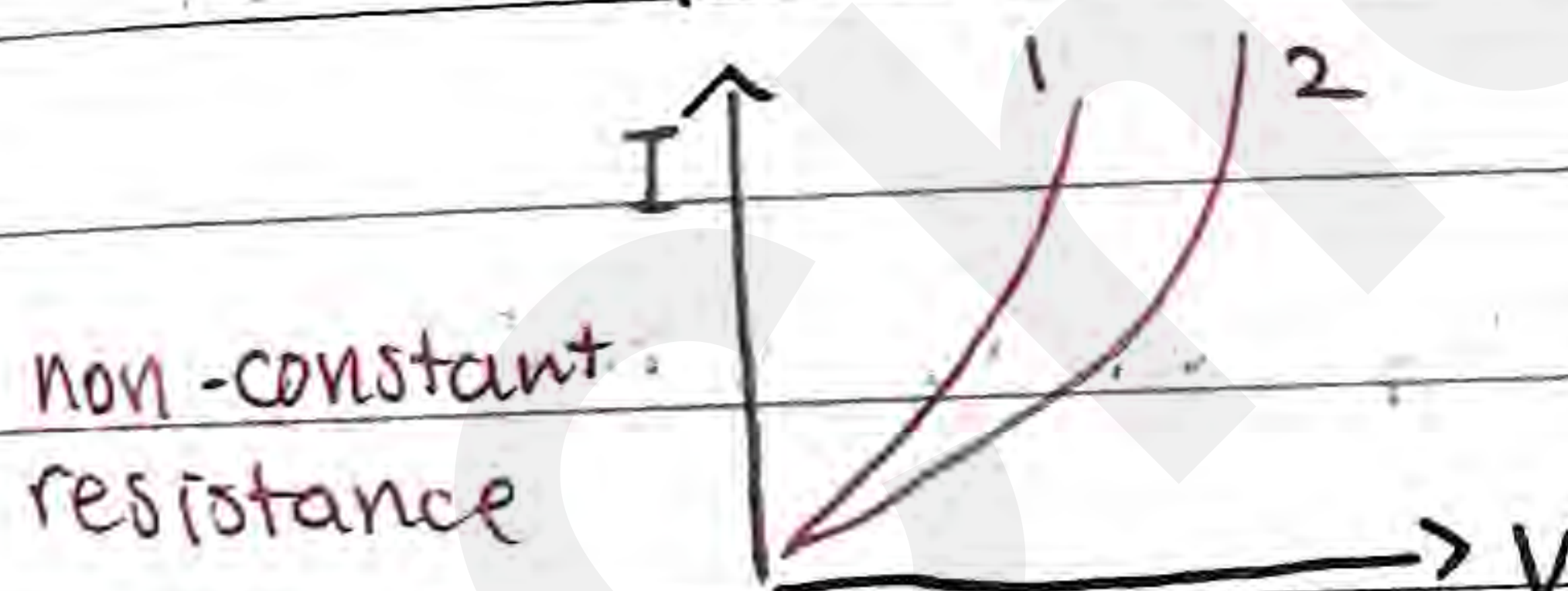However... some materials do not have a perfectly linear relation




This is a non-ohmic material
• All natural materials are non-ohmic

In circuits, everything is composed of these five components:


- | | |
|---------------------|--|
| 1. Resistor | |
| 2. Diode | |
| 3. Capacitor | |
| 4. coil / Inductors | |
| 5. Transistors | |

I-V graph

Filament (bulb)

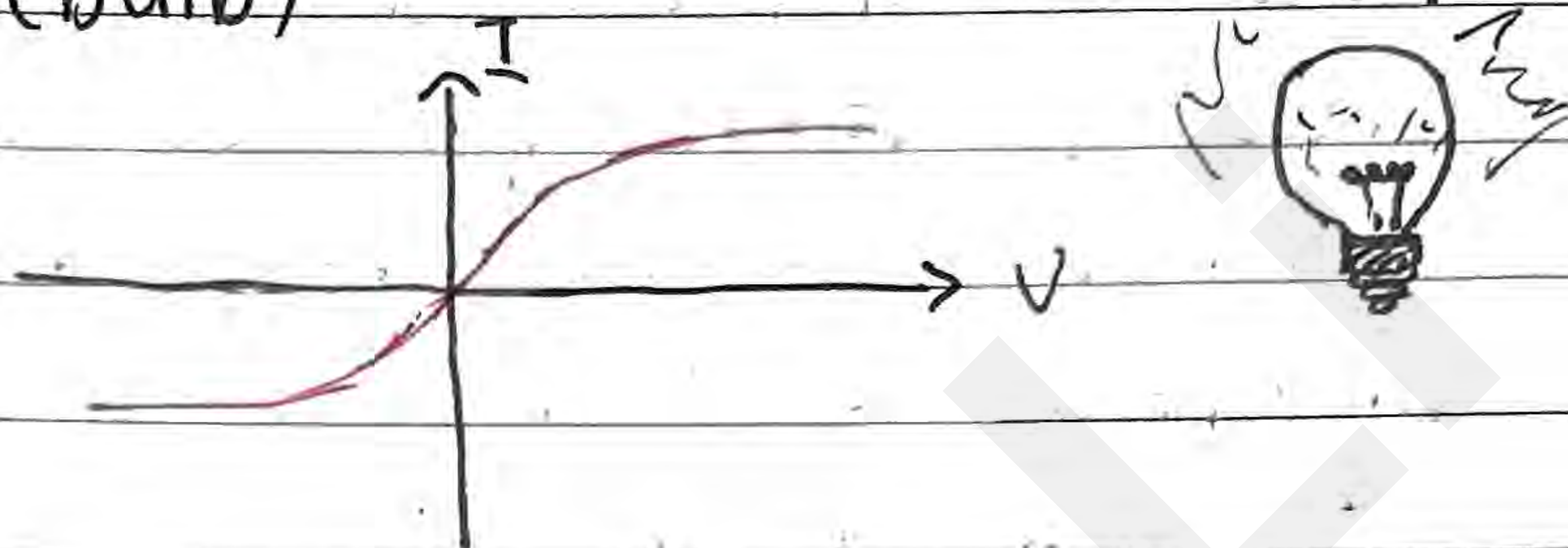

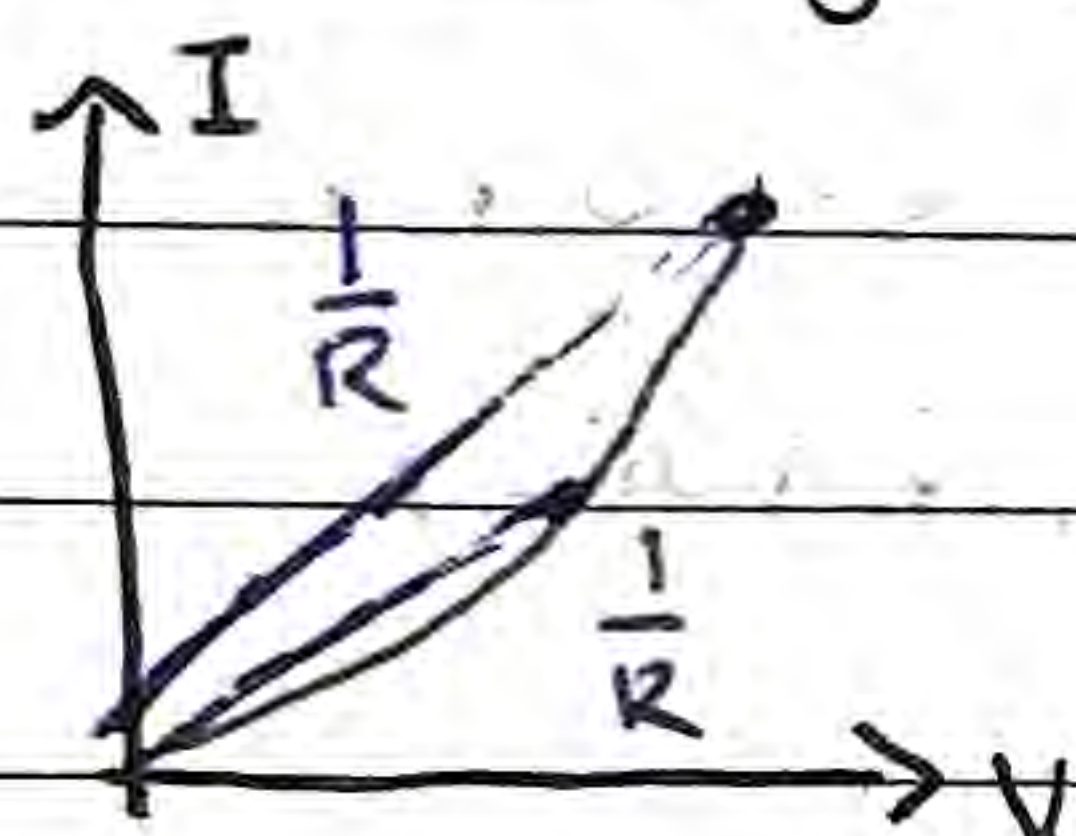In a I-V graph, resistance is NOT the slope



$$R = \frac{V}{I} \neq \frac{\Delta V}{\Delta I}$$

it's the reciprocal of the average rate of change from $V=0$. (not the instantaneous!)

Resistance is affected by various factors

The following formula illustrates this relationship

↑
for a conductor

$$R = \rho \cdot \frac{L}{A}$$

where ...

R - Resistance of object

depends on temperature →

ρ - Resistivity of material ($\Omega \cdot m$)

L - Length of object

A - Cross-sectional area

$\Rightarrow$	$R \downarrow$
$\Rightarrow$	$R \uparrow$
$\Rightarrow$	$R \downarrow$
$\Rightarrow$	$R \uparrow$

Electrical Conductivity

$$\text{Electrical Conductivity} = \frac{1}{R}$$

more resistive, less conductive


less resistive, more conductive

Temperature and resistance

As temperature increases, resistance increases.


Lower temperature, lower resistance

but at some point, resistance jumps to 0

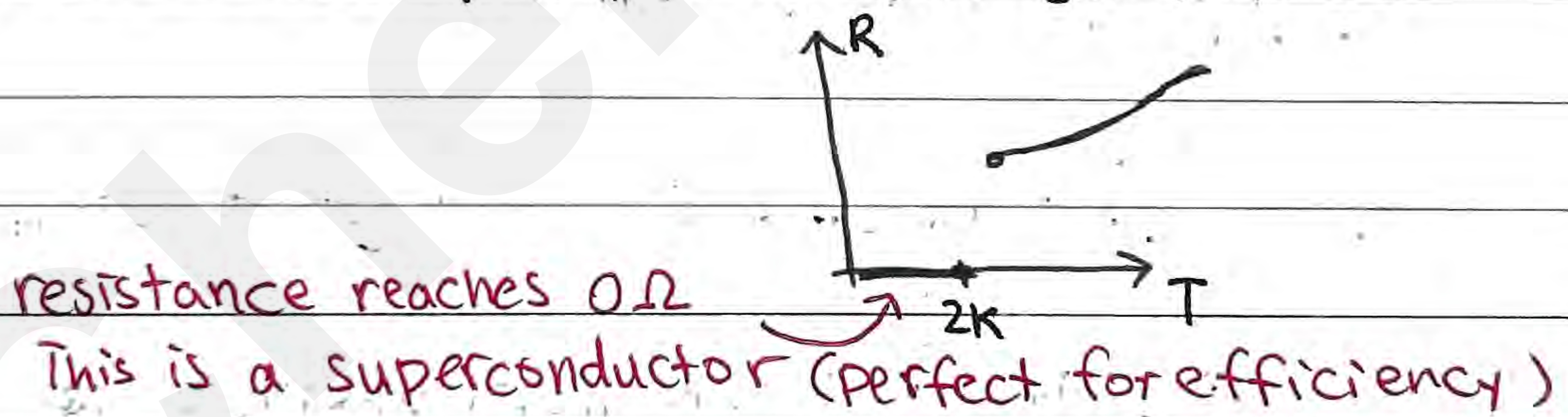

Electricity



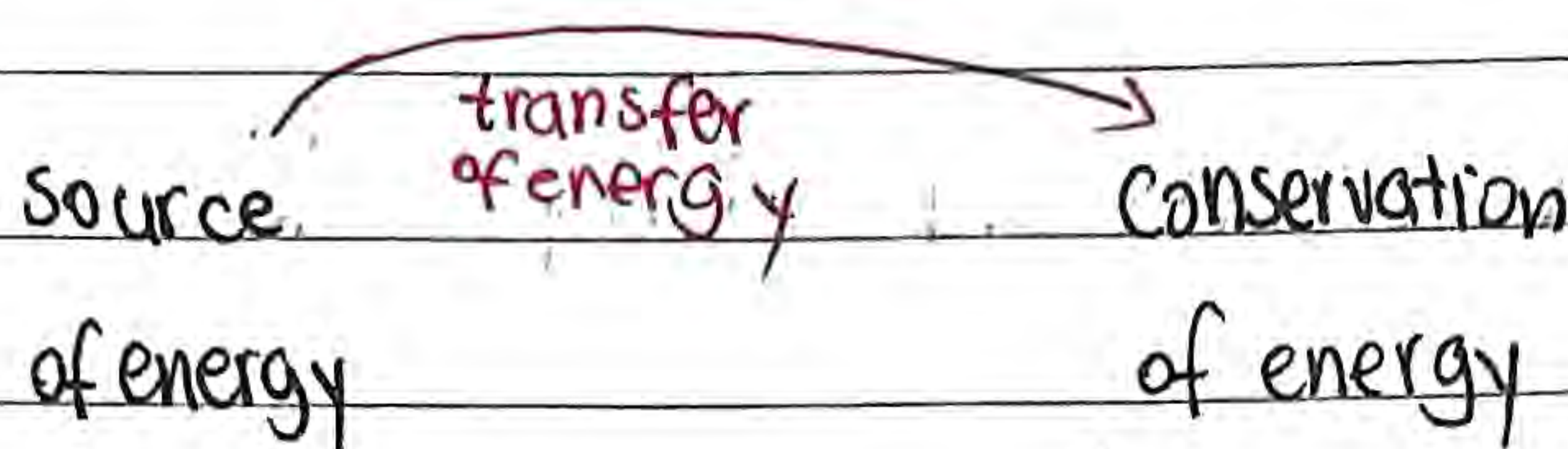
Electric circuit - To transfer energy from source to consumer



but you also need to close the loop!


In order to create a potential difference, you need a "pump" or a battery

Electric Circuit Symbols

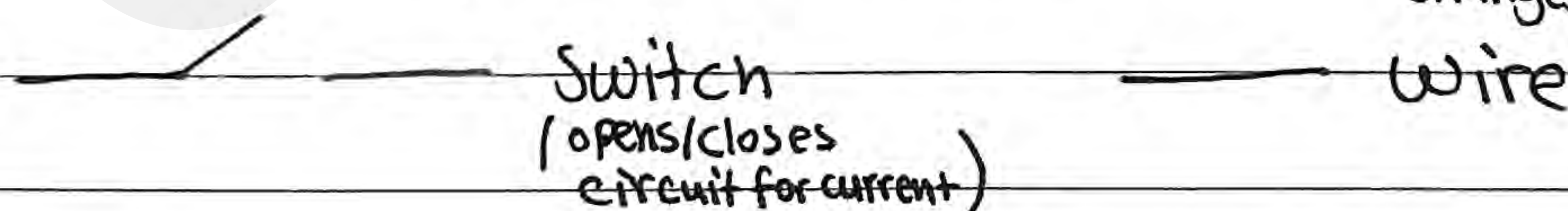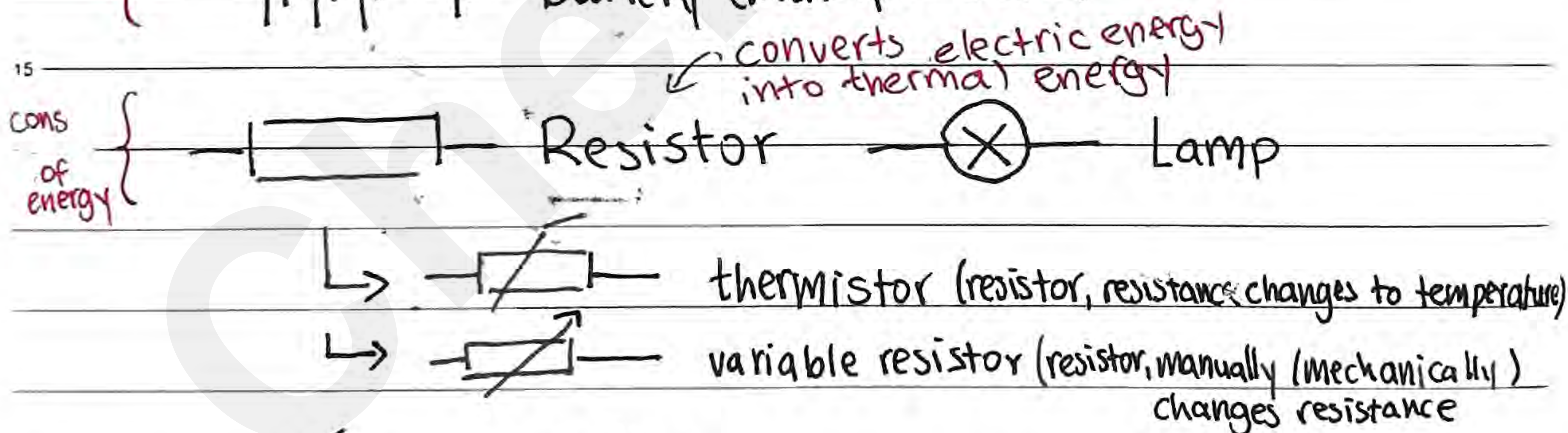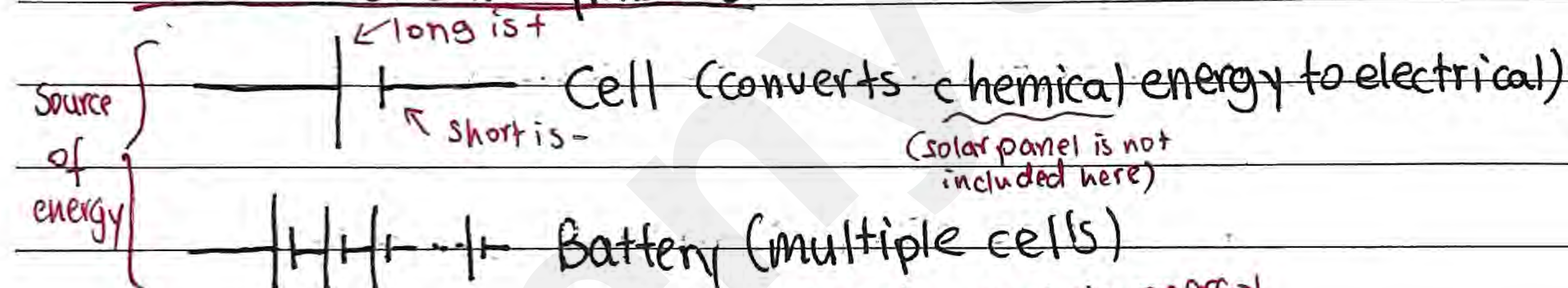

Basic Electric circuit

Open circuit

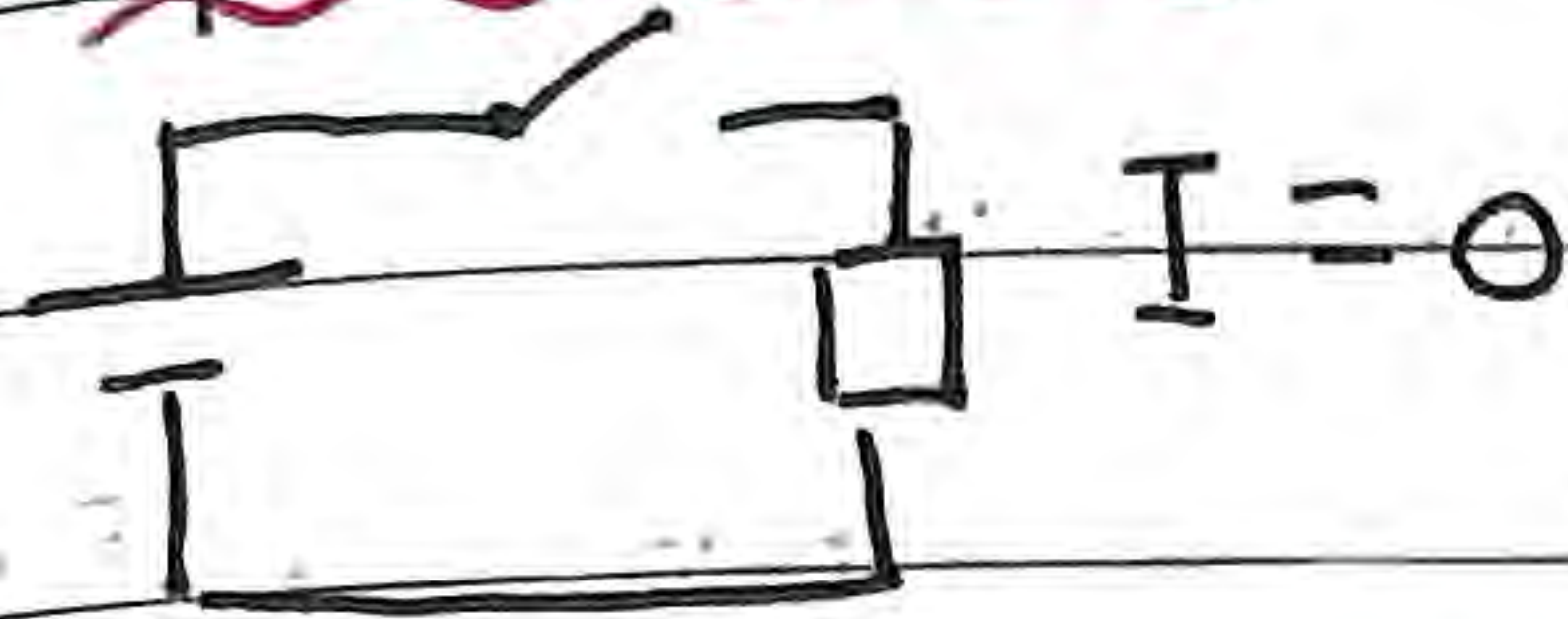


Closed circuit



opposes
flow of electron

Current is positive to
negative end

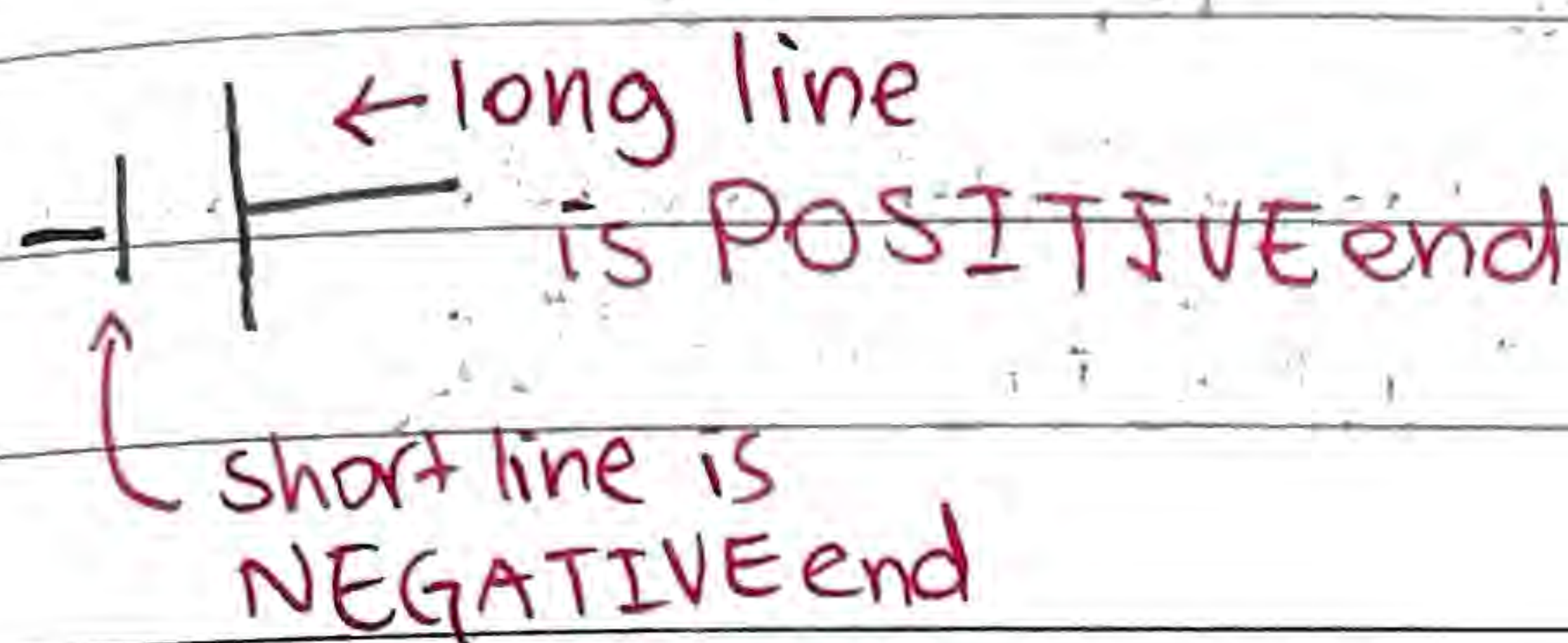

Ohm's law:

$$R = \frac{V}{I} = \frac{\text{Potential Difference}}{\text{current}}$$

E.g.  Then current = $\frac{3}{2} \text{ A} = 1.5 \text{ A}$

However, circuits are not that simple...

Resistors in series

terminals
do not
meet/
not the
same



The current through each resistor

$$\text{Equivalence Resistance} = \sum R_i$$

$$= R_1 + R_2 + R_3 + \dots$$

is the same

As such, according to Ohm's law,

$$\text{Total Voltage} = \sum V_i$$

$$= V_1 + V_2 + V_3 + \dots$$

the Potential Difference on each resistor
is not the same

Resistors in parallel



All three terminals of the resistors meet / are of the same point

• The potential difference on each resistor is the same

• The Equivalent Resistance is calculated as follows:

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_n} = \sum \frac{1}{R_i}$$

• According to Ohm's law, the current on each resistor is not the same: $I = I_1 + I_2 + I_3 \dots = \sum I_i$

You can think of it like this

In series



- Same "wire", same current
- Different terminals, different voltages

In parallel



- Different "wire", different currents
- Same terminal, same voltage

Electric Power

• You can calculate the energy passing through any component in a given amount of time

⇒ Depending on whether it is source or consumer of energy, it will be power released or absorbed respectively


total power
= $\sum P_i$
(for both series, parallel)

$$P = I^2 \cdot R = V \cdot I$$

where...

$$\hookrightarrow V = I \cdot R$$

$$P = \frac{V^2}{R}$$

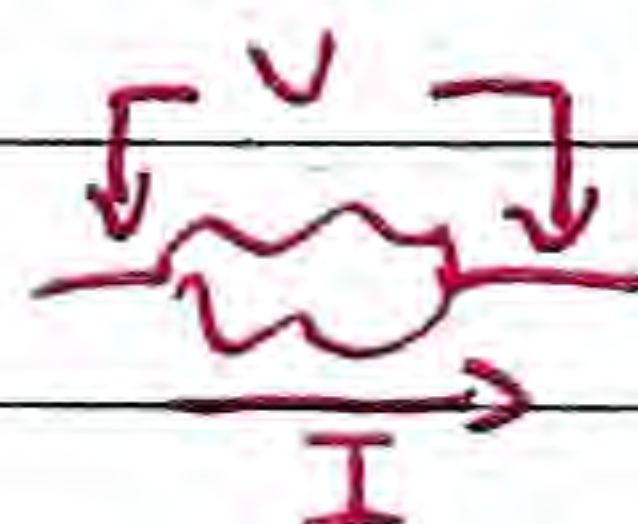


P - Electric power of component

R - Resistance of component

I - Current passing through


V - Potential difference of terminals

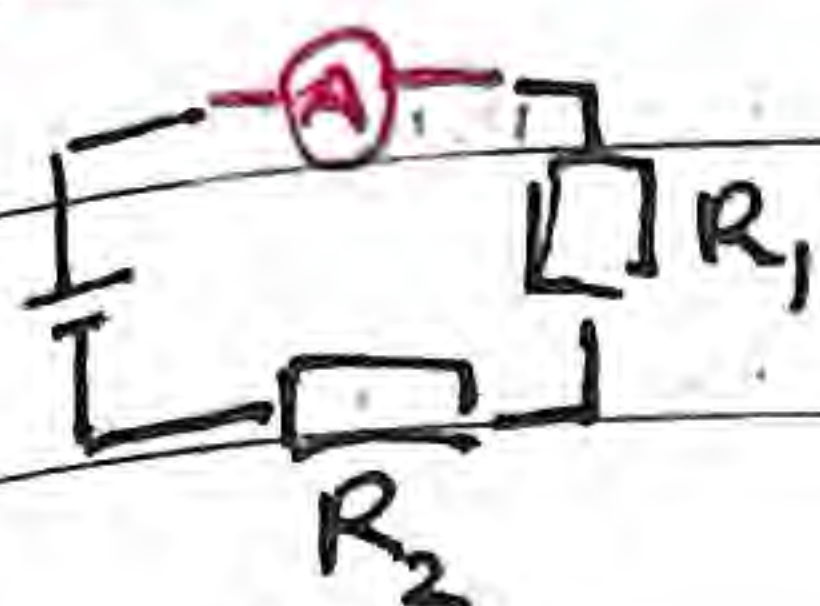Ideal Ammeter - An instrument measuring the current in a series such that the resistance is negligible



↳ to allow for all current to pass through ammeter

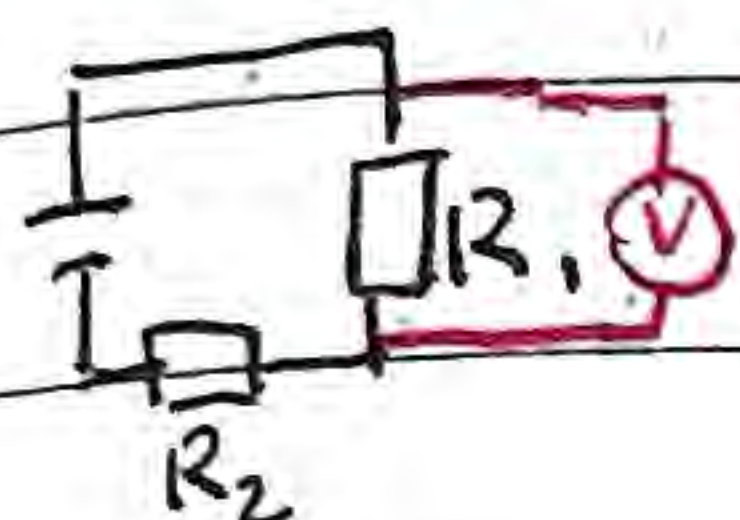Ideal Voltmeter - An instrument measuring the potential difference in parallel such that the resistance is infinitely large






↳ to prevent current from escaping to voltmeter

Complex circuits often consist of in series and in parallel components

↳ You can group these different components to do mini calculations

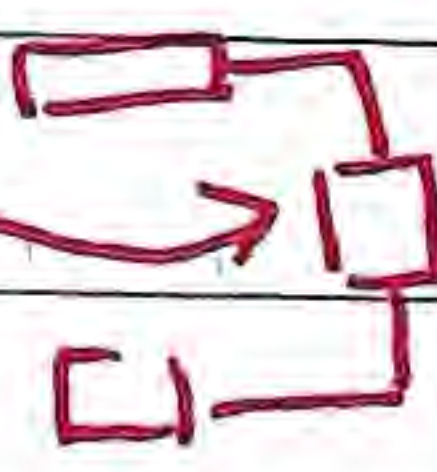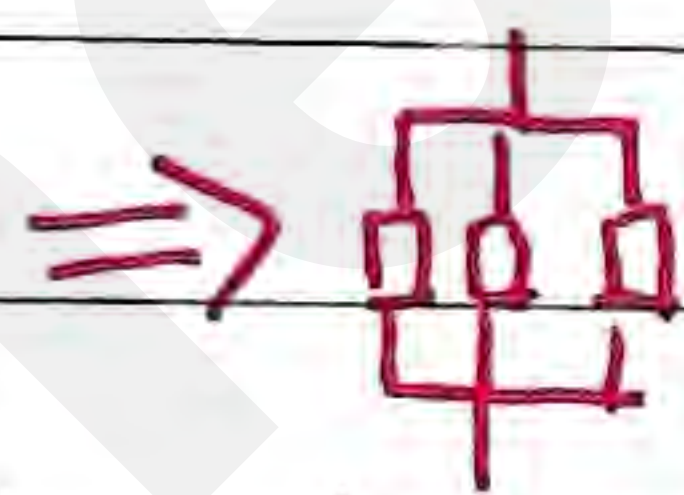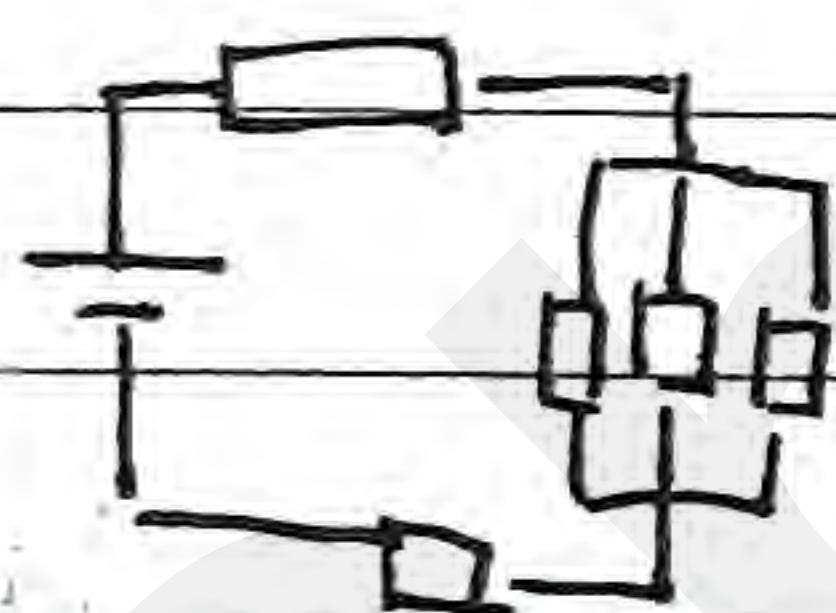(go from innermost circuit, the one you're 100% certain with, of the same type)





to then calculate R_{eq} for overall circuit

After you find current of entire circuit, you go inwards one-by-one

Analyzing parallel and series circuits

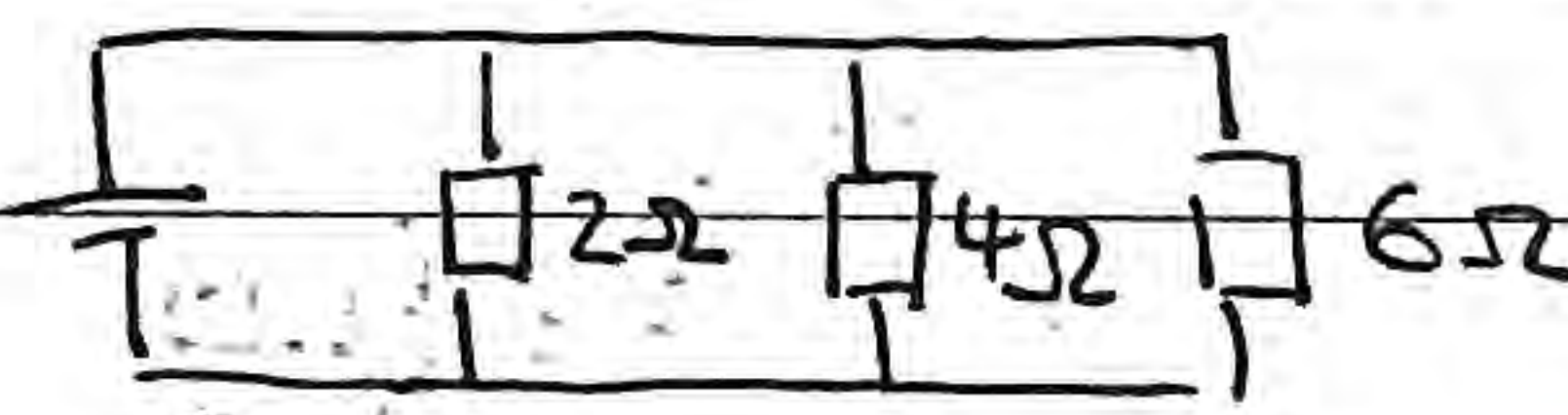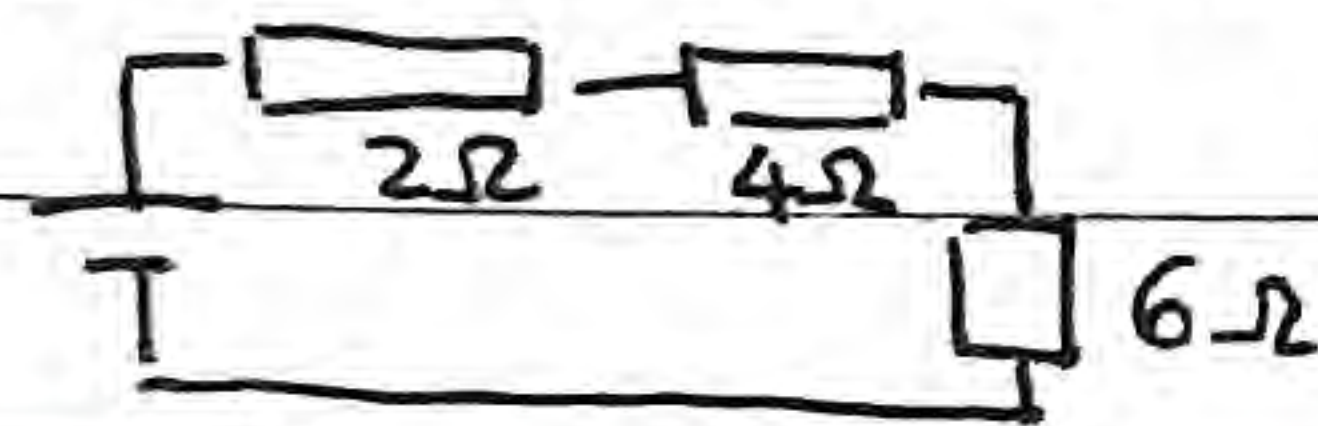E.g. For 24V circuit with resistors of 2Ω , 4Ω , 6Ω



R_{eq} lower for parallel, greater current, greater power (useful for high power)

R_{eq} higher for series, lower current, lower power (useful for low power)

Types of resistors

> Thermistor - Temperature dependent resistance

 • As temperature increases, resistance decreases.

> Light dependent resistor - Intensity of light dependent resistance


 (LDR)

• As intensity of light increases, resistance decreases

> Potentiometer - Length dependent resistance

 • As length of resistor increases, resistance increases

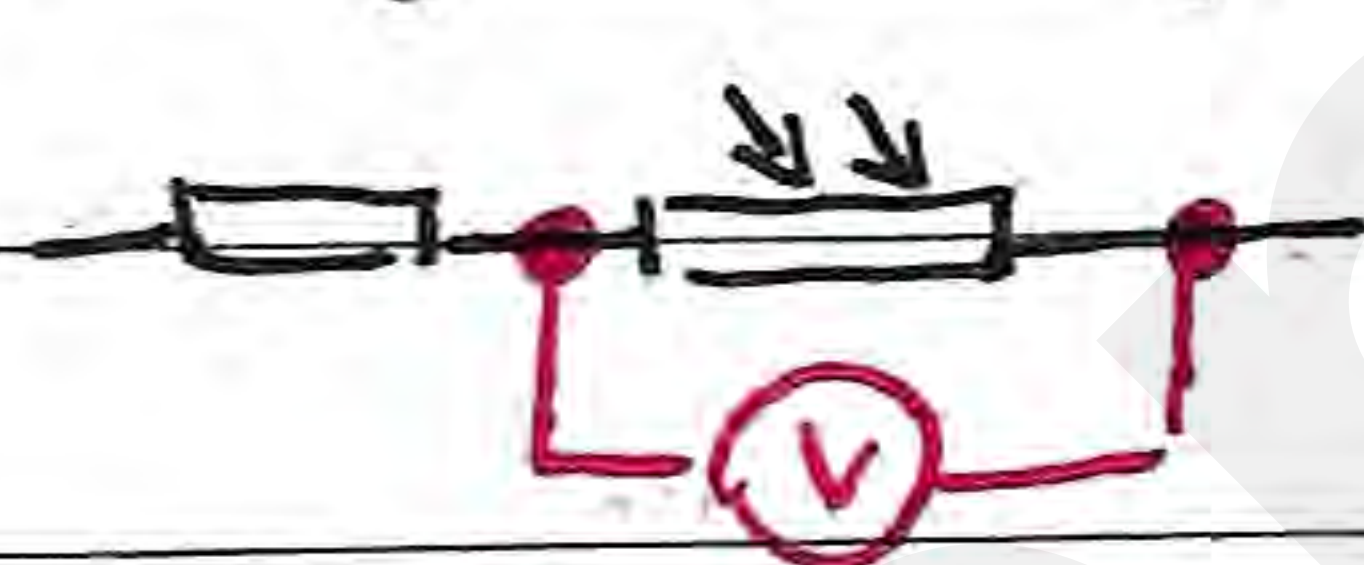E.g. Given constant current, what happens to measured voltage as light intensity increases



$I \uparrow$ thus $R \downarrow$

Given $V = I \cdot R$

$V \propto R \rightarrow R \downarrow$ so $V \downarrow$

Voltage, current, resistance

• As we know, voltage stays constant in a circuit connected in parallel, current stays constant in a circuit connected in series.

• As such, we can also get the following formula...

$$V = IR$$

$$\Rightarrow \frac{V_1}{V_2} = \frac{I_1 \cdot R_1}{I_2 \cdot R_2}$$


For constant voltage (parallel)

For constant current (series)

$$\frac{I_2}{I_1} = \frac{R_1}{R_2}$$

$$\frac{V_1}{V_2} = \frac{R_1}{R_2}$$

Can be useful when one resistance is equivalence resistance

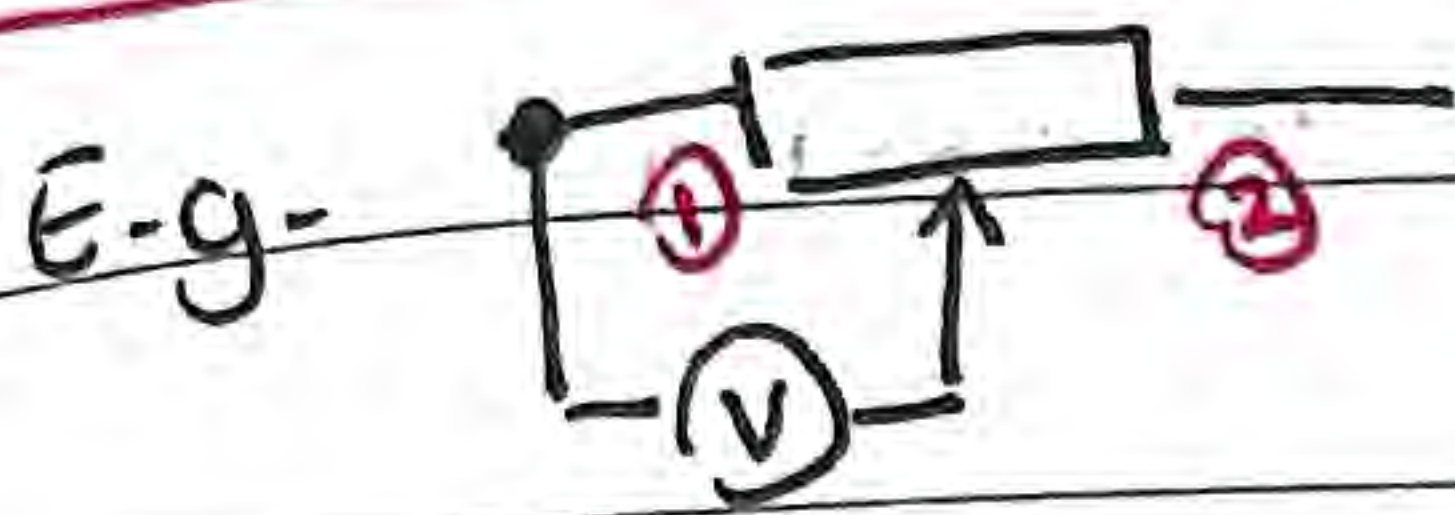Potentiometer



the labelled resistance is the maximum resistance

At ①, voltmeter does not measure a potential difference, $V = 0$

At ②, voltmeter measures maximum potential difference

Voltage, current, resistance

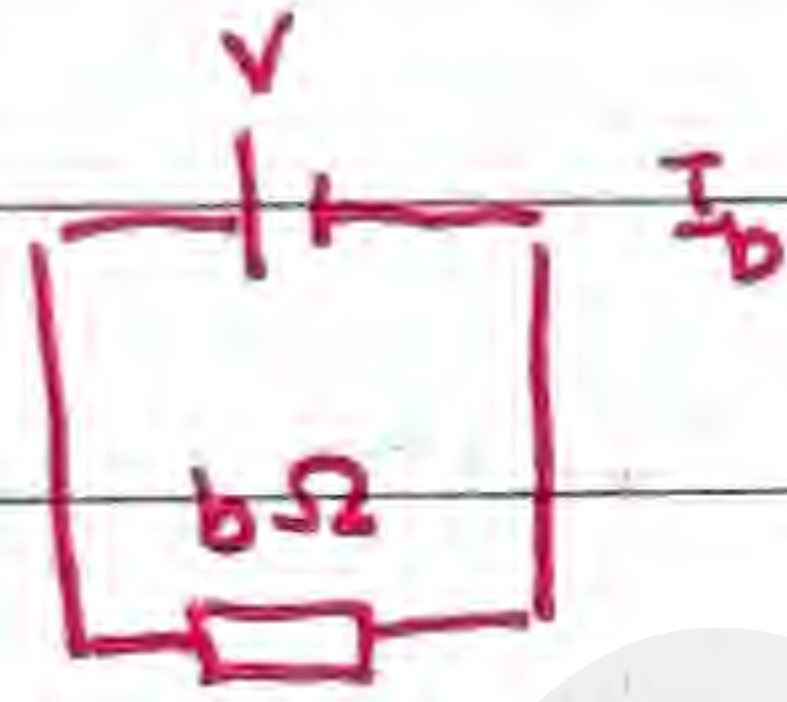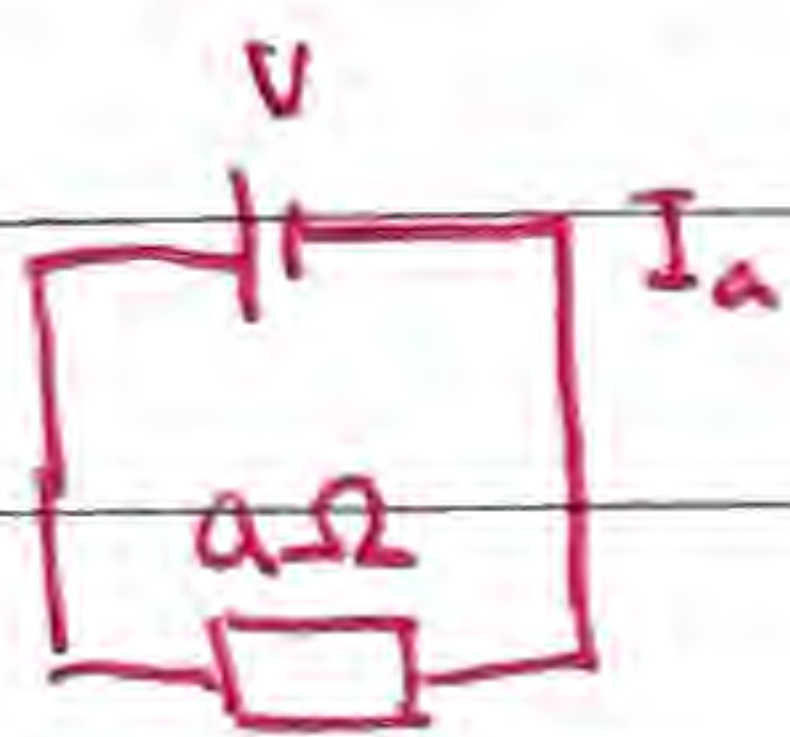When resistance changes in a circuit, so will the current (assuming voltage is constant due to cell)




if $b > a$, then $I_b < I_a$

So, when a problem requires a change in resistance, make sure to recalculate the current

↳ To find voltage, power, etc.

Power consumed = Power delivered

$$\sum P_i \text{ of individual circuits} = \text{Power of system} = I \cdot V$$

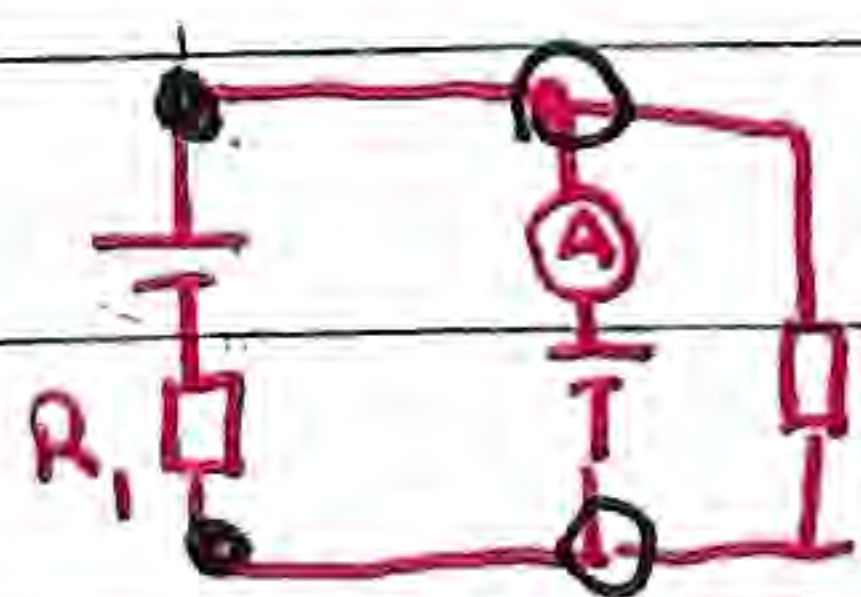Multiple cell battery

two terminals are connected in parallel, V is same

You know V of cell is $6V$, but not

↳ R_1 must have $0A$ passing through ← this also $6V$ ← ∴ (since there's resistance)


or else would decrease (taken out)

Complicated electric circuits

• Remember an ideal voltmeter has ∞ resistance


• And, when...

$$V = 0 \text{ V}$$

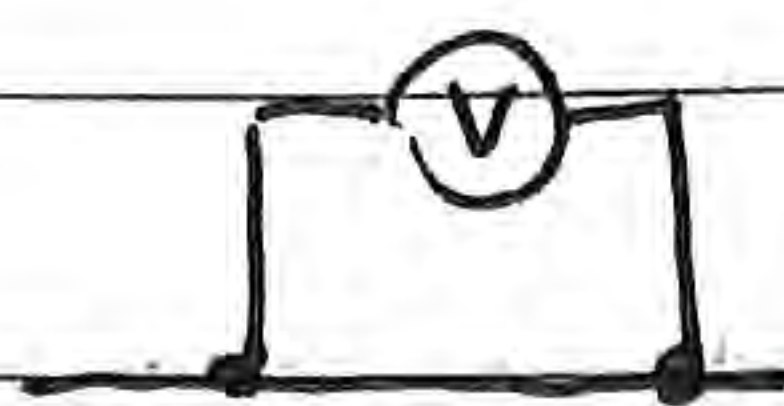

is the same as no resistor in between

then... E.g.

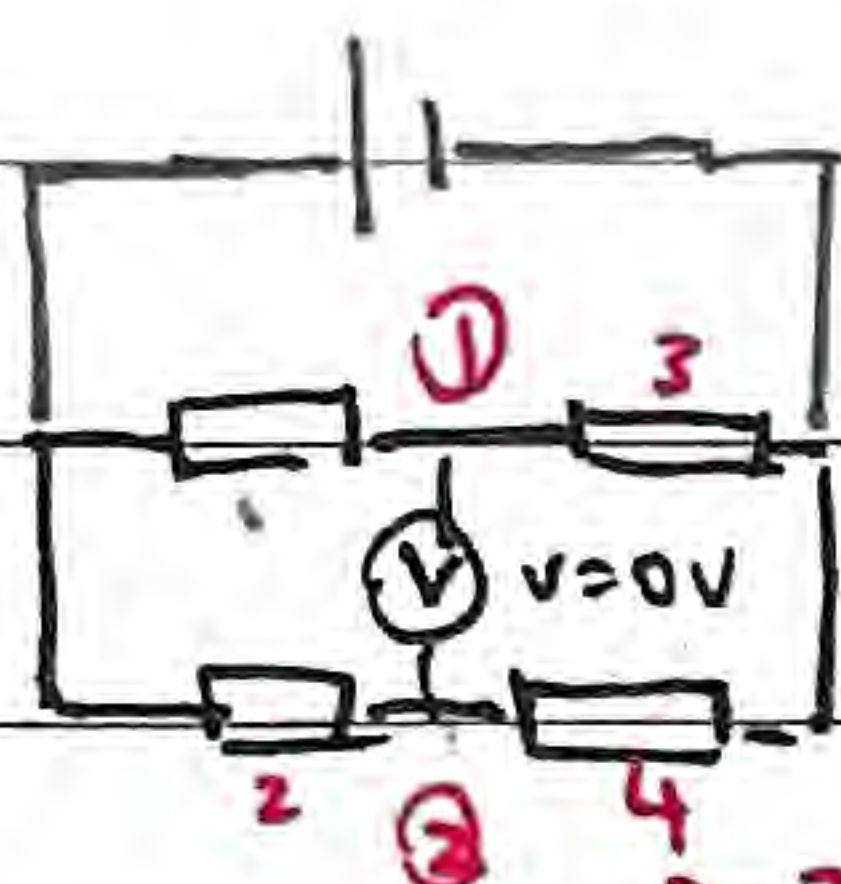

$V=0$ so energy from cell to ① is same as to ③

$R=?$ thus $V_1 = V_2$, $V_3 = V_4$

but also, voltmeter allows no current to pass through, so $I_3 = I_1$ (no splitting), $I_4 = I_2$

thus

$$\frac{V_1}{V_2} = \frac{V_3}{V_4} \Rightarrow \frac{I_1 R_1}{I_2 R_2} = \frac{I_3 R_3}{I_4 R_4}$$

Electromotive Force (Emf, $\mathcal{E}$)


→ Not force, it's energy

The work done per unit charge in moving a charge from one terminal of the battery to the other.

↳ the units are volts, but it's not the same as electrical potential difference.

Internal Resistance

Recall a battery...

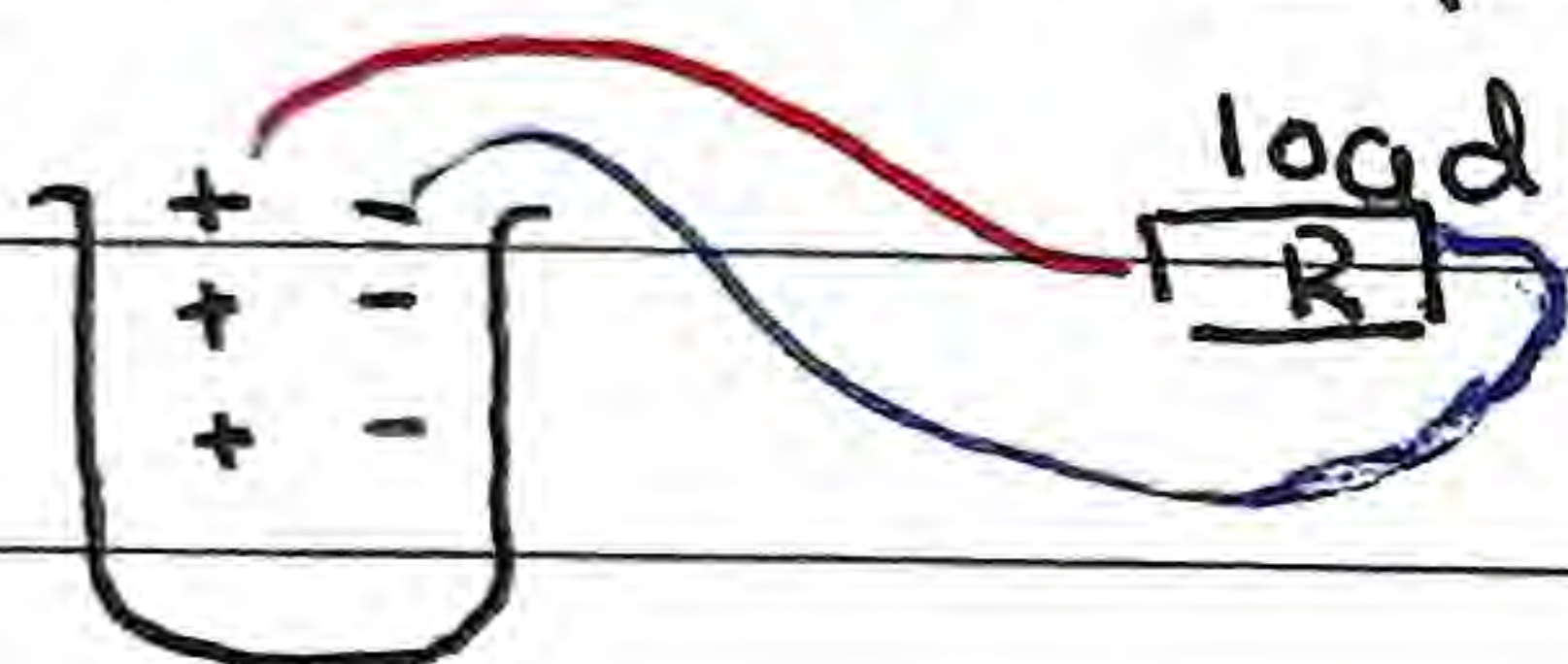

since charges must travel through a medium (non-vacuum)

Thus we can think of it like this...



Real Battery

Ideal Battery



$\mathcal{E}$ is the voltage of an ideal battery and the voltage of a real battery when current = 0 (open circuit)

↳ Thus actual voltage of a real battery in a closed circuit will never reach $\mathcal{E}$ (advertized voltage)



$$\text{current} = \frac{\mathcal{E}}{R+r}$$


$$\mathcal{E} = I(R+r)$$

$$\text{Voltage} = \mathcal{E} - Ir$$


↑
energy taken out

Measuring internal resistance

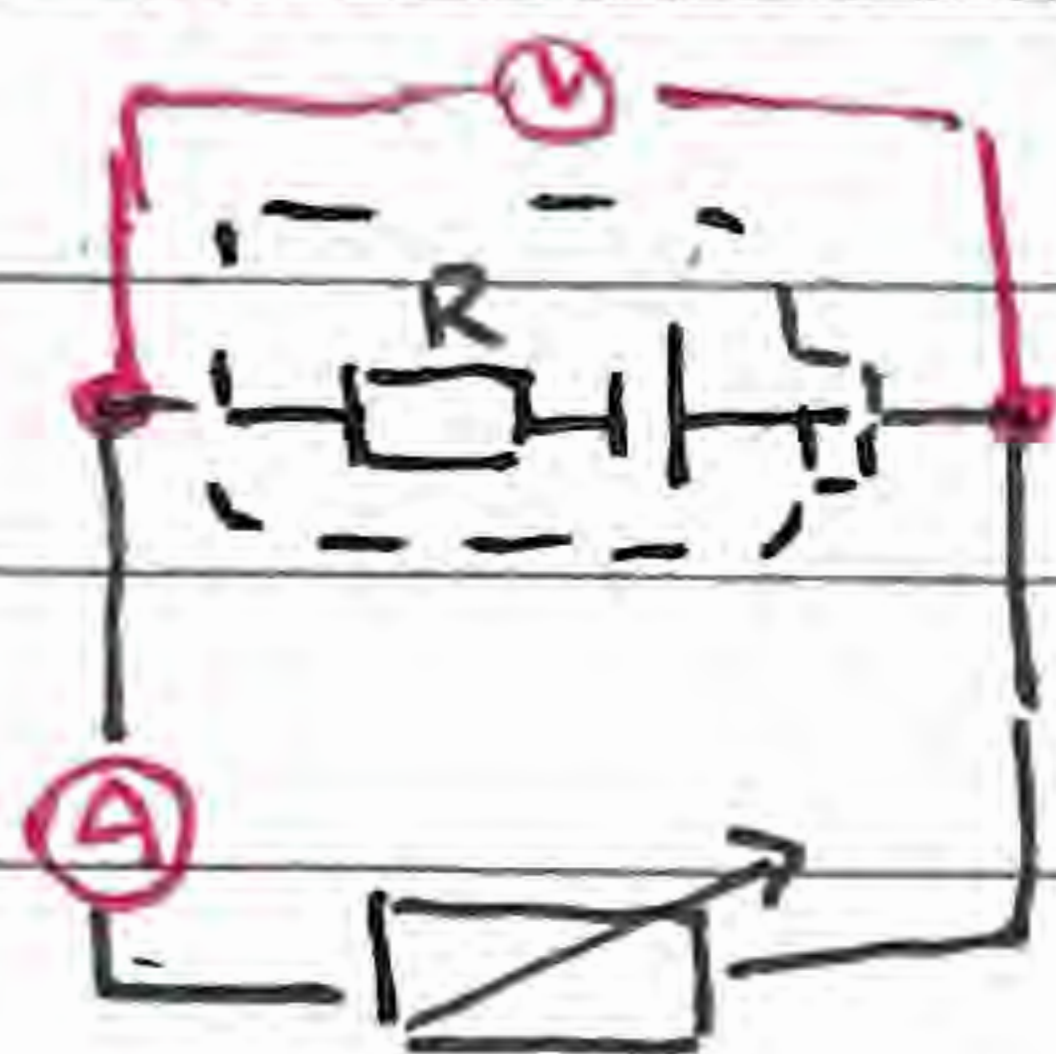- You can measure internal resistance by changing external resistance and measuring current and electrical potential difference



I vs V

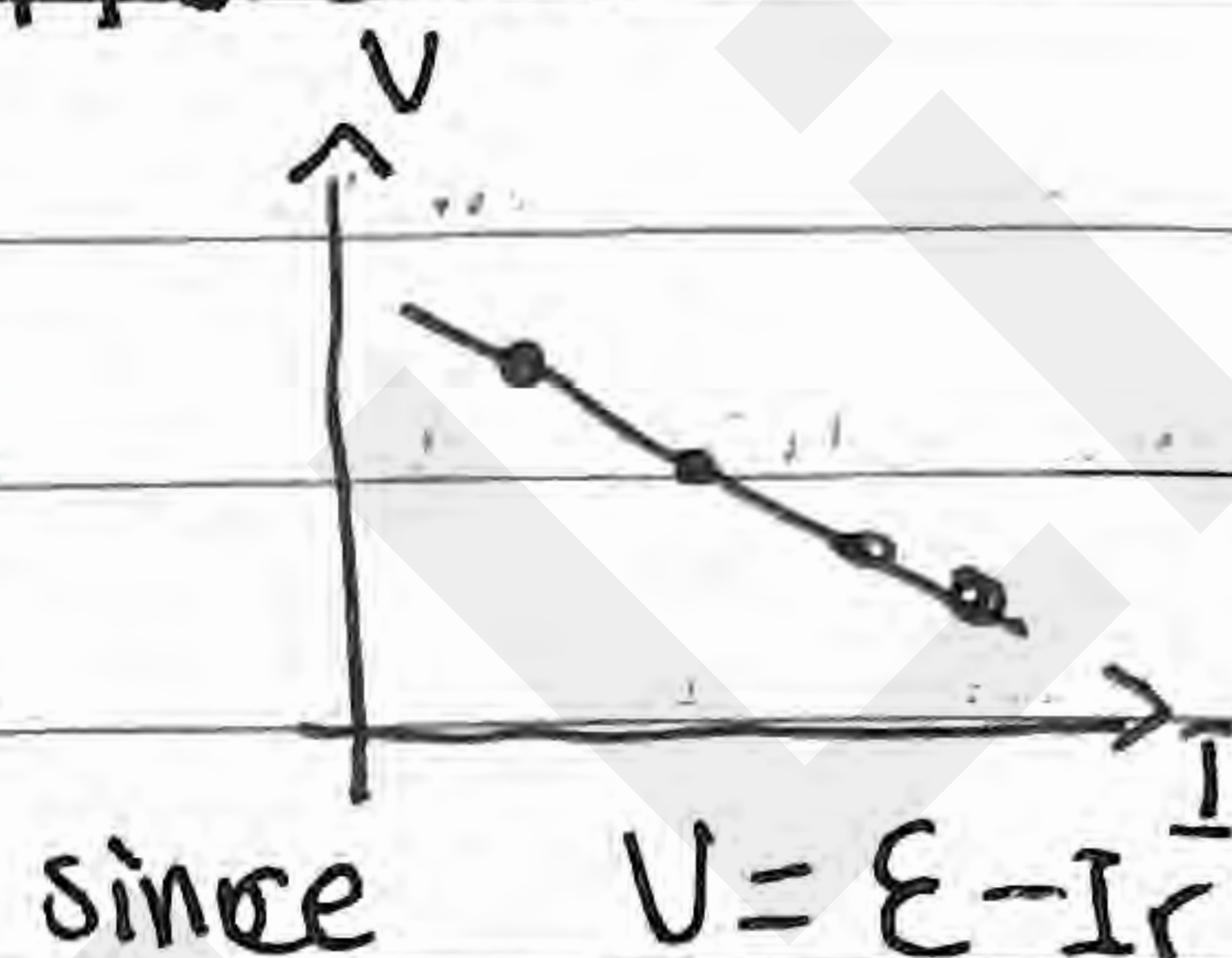

so $\bar{E}mf$ is y-intercept, internal resistance is slope